


IIT INDORE

EMPEL PROJECT


Presented By :
GROUP E1-B4

Aditi Luniya - 230002003
Ayush Jindal - 230002014
Harshvardhan - 230002027
Kshithij Singhanian - 230002035


MATLAB SIMULATION

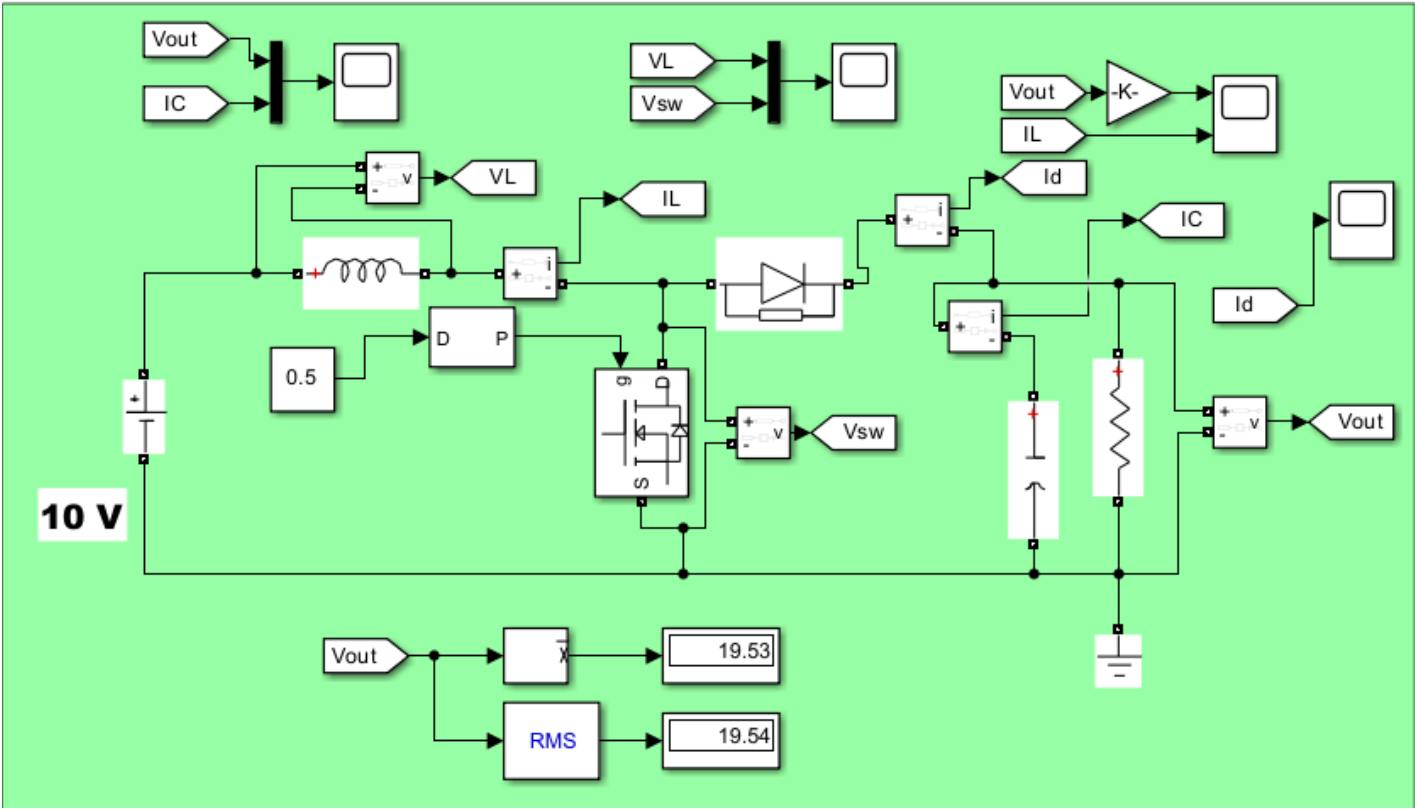


VOLTAGE ACROSS INDUCTOR

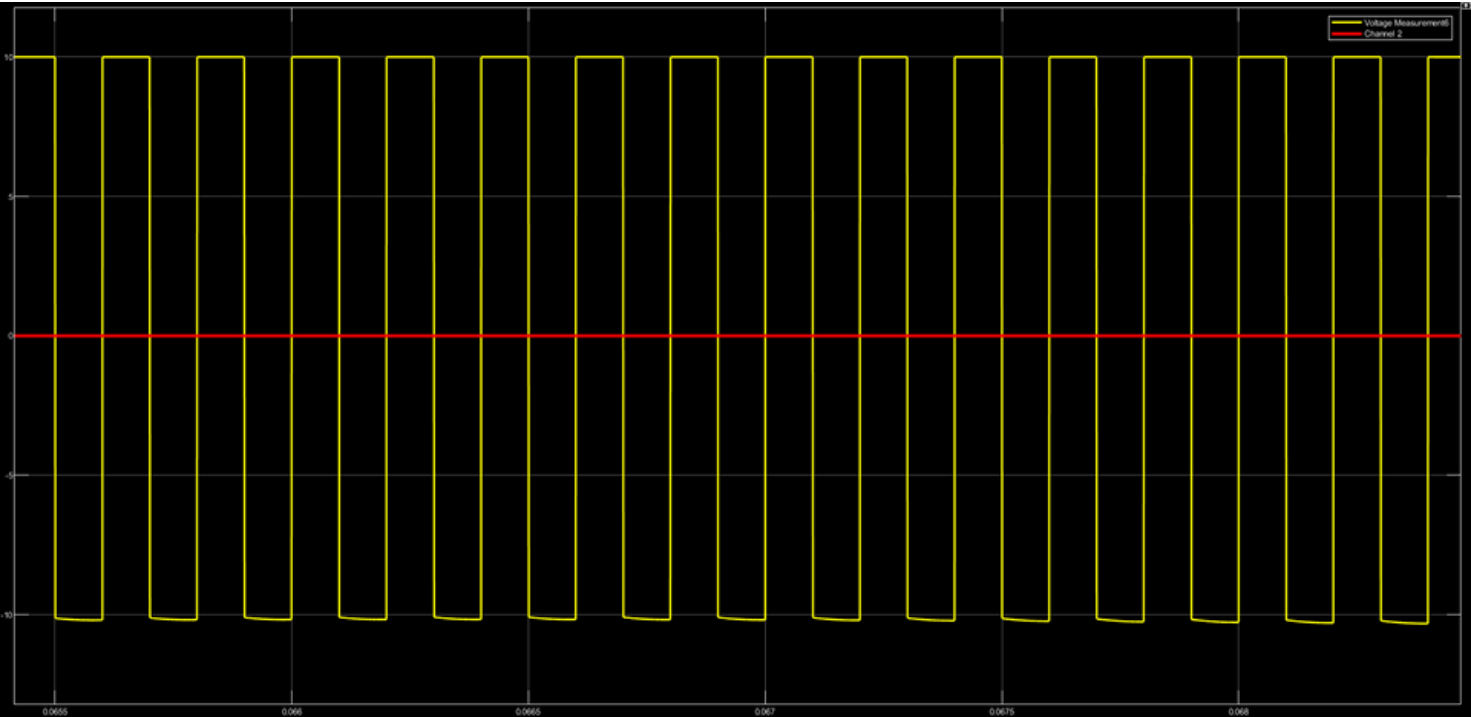


CURRENT THROUGH DIODE

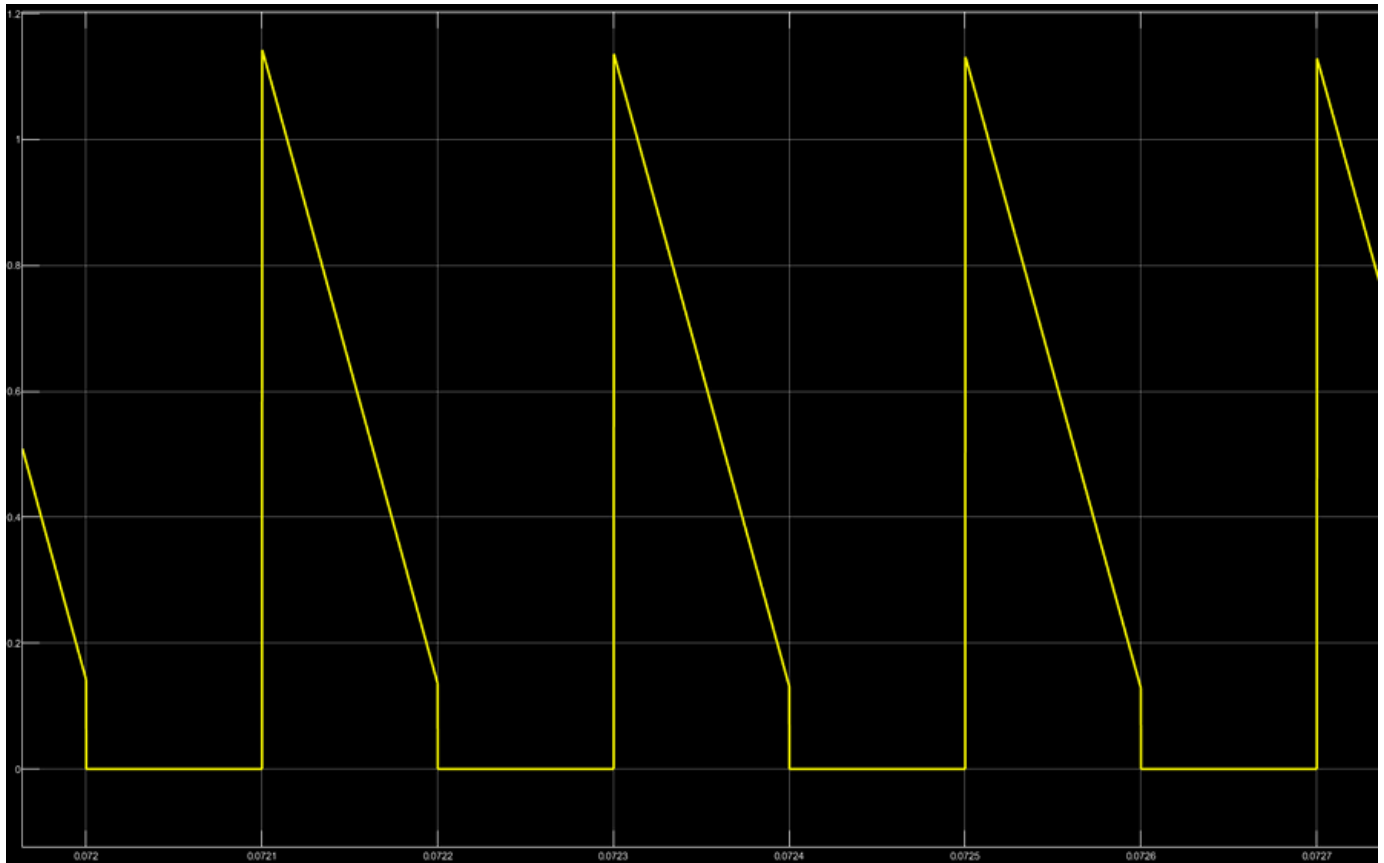

PRACTICAL WAVEFORMS.

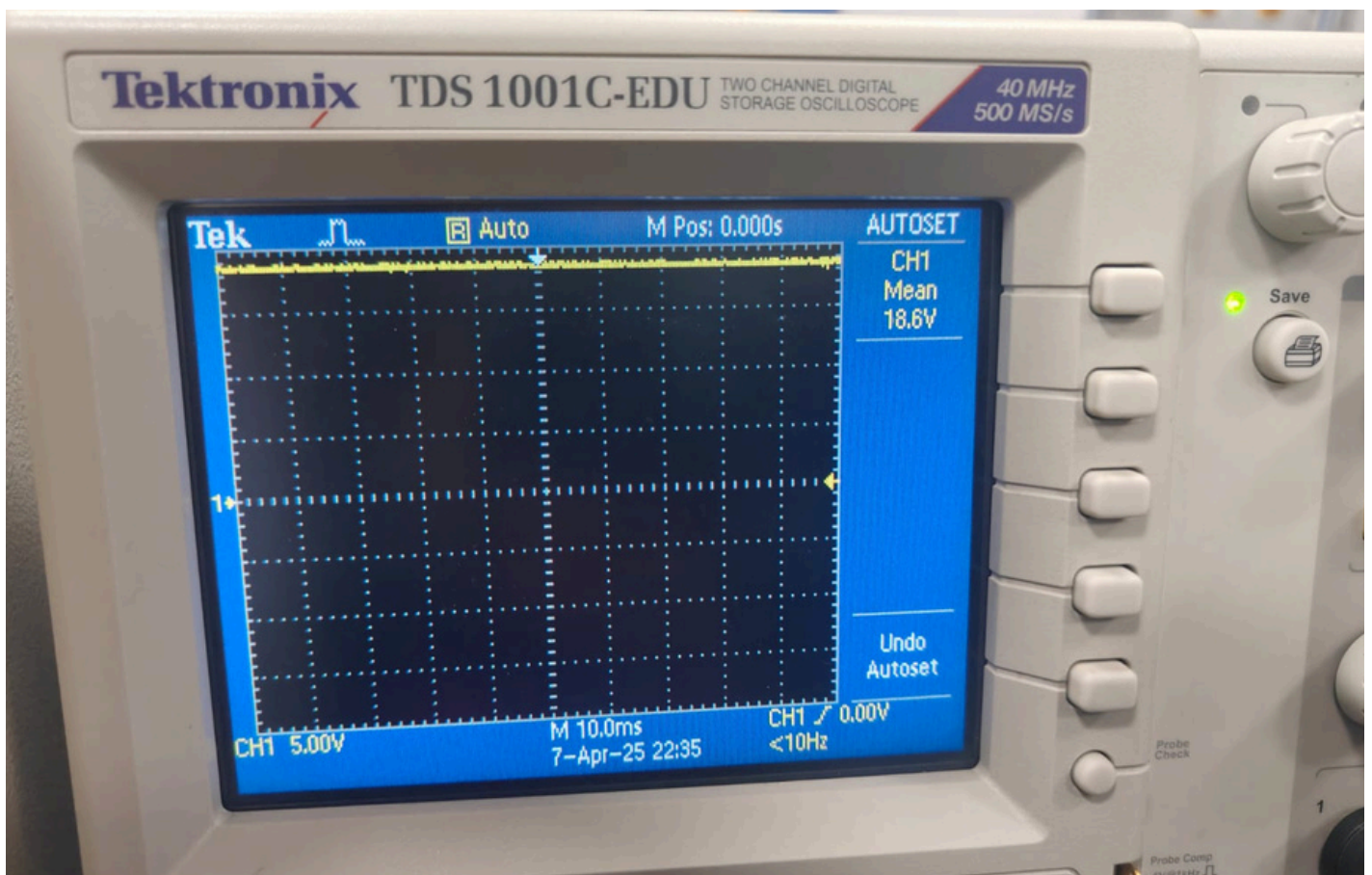

VOLTAGE ACROSS INDUCTOR

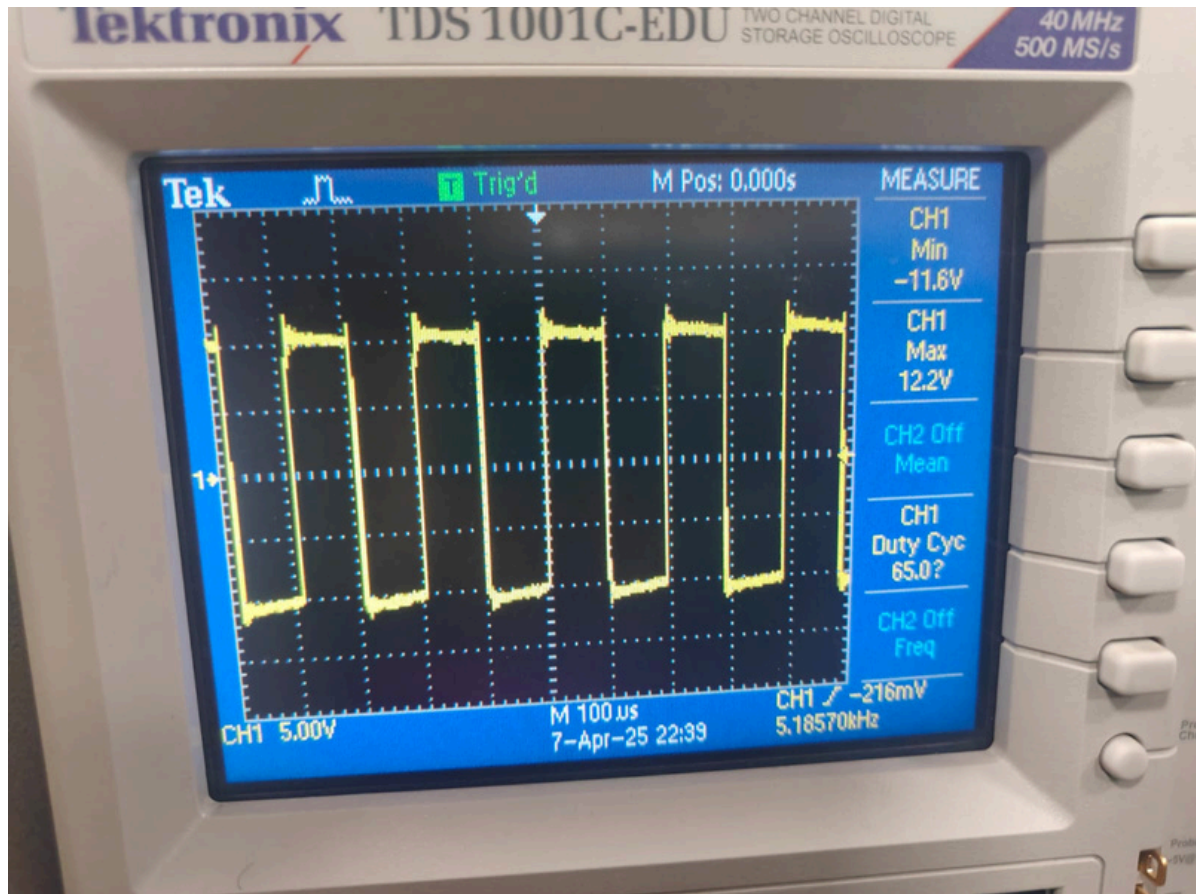

CURRENT THROUGH DIODE

